

EE315 - Electronics Laboratory

Experiment 4

BJT Small Signal Analysis

Preliminary Work

1.a) Calculate A_v , A_i , R_{in} , and R_{out} on the circuit given in Figure 1. Assume that C_{Ci} and C_{Co} behave as open circuit for DC signals and as short circuit for AC signals.

1.b) Determine limits of the signal source, v_s , for the transistor to remain in forward-active region.

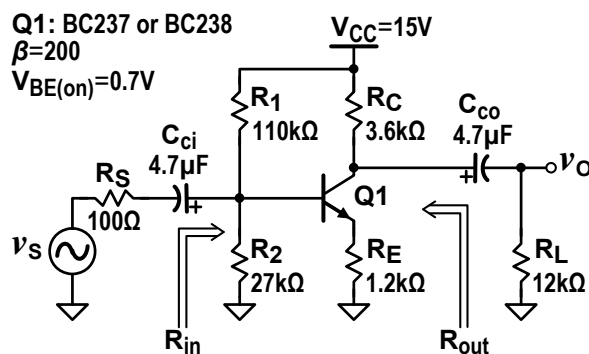


Figure 1. Common-emitter amplifier

2.a) Calculate A_v , A_i , R_{in} , and R_{out} on the circuit given in Figure 2. Assume that the coupling capacitors, C_{Ci} and C_{Co} , behave as open circuit for DC signals and as short circuit for AC signals.

2.b) Determine limits of the signal source, v_s , for the transistor to remain in forward-active region. (Hint: AC current on R_L will be added onto the quiescent emitter current.)

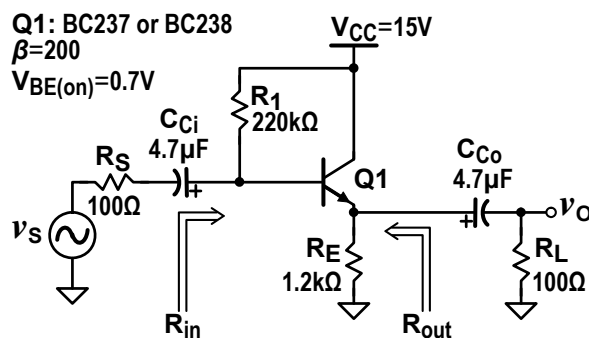


Figure 2. Common-collector amplifier
(emitter follower)

Procedure

1. Build the circuit given in Figure 1. Use the function generator to obtain **1 V_{p-p}**, **1 kHz** as **v_s**. Note the polarity of the capacitors on the circuit diagram.

1.a) Measure the voltage gain, **A_v**. Use the oscilloscope in X-Y mode, probing **v_s** on Ch-1 (X) and **v_o** on Ch-2 (Y).

$$V_{Sp-p} = \quad V_{Op-p} = \quad A_v =$$

1.b) Determine the current gain, **A_i**, by measuring the peak-to-peak AC voltages across **R_S** and **R_L**.

$$V_{RSp-p} = \quad V_{RLp-p} =$$

$$I_{Sp-p} = \quad I_{Lp-p} = \quad A_i =$$

1.c) Disconnect **R_L** and measure the input resistance, **R_{in}**. Use the oscilloscope in X-Y mode, probing **i_s** (voltage across **R_S**) on Ch-1 (X) and **v_s** on Ch-2 (Y). Note that, the two oscilloscope channels must share a single, common node for proper ground connection.

$$V_{Sp-p} = \quad V_{RSp-p} = \quad I_{Sp-p} = \quad R_{in} =$$

1.d) Measure peak-to-peak output voltage while **R_L** is disconnected. Connect a **4.7 kΩ** variable resistor in place of **R_L**, and adjust the variable resistor to obtain half the output voltage measured without any load. Measure the value of variable resistor that will give the **R_{out}** of the amplifier.

$$V_{Op-p(NoLoad)} = \quad R_{out} =$$

1.e) Find the maximum peak **v_s** amplitudes before the transistor goes into cut-off or saturation. Compare the results with your calculations in the preliminary work.

$$V_{S\text{peak}(cut-off)} = \quad V_{S\text{peak}(sat)} =$$

1.f) Connect a **4.7 μF** capacitor in parallel to **R_E**. Make sure that the polarity of the capacitor matches the DC voltage polarity on **R_E**. Measure the voltage gain, **A_v**, again as described in step 1.a.

$$V_{Sp-p} = \quad V_{Op-p} = \quad A_v =$$

1.g) Draw the small signal model of the common-emitter amplifier with the capacitor in parallel to **R_E**, and calculate the voltage gain, **A_v**, based on your model.

2. Build the emitter-follower circuit given in Figure 2. Verify that the function generator output is still set to **1 V_{p-p}**, **1 kHz**, and repeat the steps **1.a**, **1.b**, and **1.c**.

2.a) Measure the voltage gain, **A_v**.

$$V_{Sp-p} = \quad V_{Op-p} = \quad A_v =$$

2.b) Determine the current gain, **A_i**.

$$V_{RSp-p} = \quad V_{RLp-p} =$$
$$I_{Sp-p} = \quad I_{Lp-p} = \quad A_i =$$

2.c) Disconnect **R_L** and measure the input resistance, **R_{in}**.

$$V_{Sp-p} = \quad V_{RSp-p} = \quad I_{Sp-p} = \quad R_{in} =$$

2.d) Increase **v_s** amplitude to **2.0 V_{p-p}** and observe **v_O** on the oscilloscope. How do you explain the distortion in the **v_O** waveform?

2.e) Find a way to restore the **v_O** waveform while keeping **v_s** amplitude at **2.0 V_{p-p}**, and **R_L = 100 Ω**. Explain how you can restore the **v_O** waveform.

2.f) Set the function generator output back to **1 V_{p-p}**, and measure the output resistance, **R_{out}**. You should use a smaller variable resistor such as **100 Ω** to obtain a better precision with emitter-follower. Make sure that the output waveform is not distorted while you measure **R_{out}**.

$$V_{Op-p(NoLoad)} = \quad R_{out} =$$