

## EE203 - Electrical Circuits Laboratory

# Experiment - 9

## Feedback Circuits

### Objectives

1. Observe operation of simple voltage regulator and oscillator circuits with feedback configurations.

### Preliminary Work


1. Consider the voltage regulator on the right.

**1.a)** Determine the zener voltage  $V_Z$  to obtain **4 V DC** output.

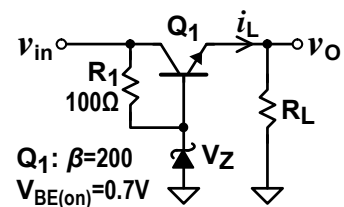**1.b)** Simulate the designed circuit.

Measure line regulation when  $v_{in}$  has **+/-0.5V** variation around **6.0 V DC**. Repeat line regulation measurement when DC value of  $v_{in}$  is **8.0 V**.

Measure load regulation when  $i_L$  changes from **0.4 mA** to **100 mA** for  $v_{in} = 6.0V$  and  $v_{in} = 8.0V$ .




2. Consider the **Wien bridge oscillator** on the right.

**2.a)** Express the oscillation frequency in terms of circuit parameters.

**2.b)** Determine  $R_1$  and  $R_2$  to obtain **16 kHz** oscillation frequency when  $C_1 = C_2 = 1 \text{ nF}$ .

**2.c)** Describe the oscillation criterion and determine  $R_3$  accordingly when  $R_4 = 10 \text{ kΩ}$ .

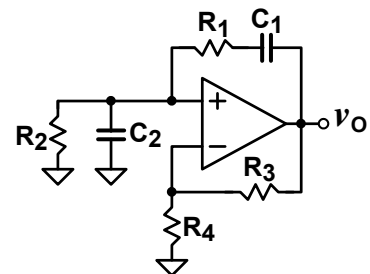**2.d)** Simulate the designed circuit by using **AD795** opamp model with **+/-12 V** supplies. Change  $R_2$  and plot the oscillation frequency as a function of  $R_2$ .




3. Consider the **Schmitt trigger oscillator** on the right.

**3.a)** Determine the value of  $R_3$  to obtain **4 Vp-p** amplitude at  $v_n$ . Assume that  $v_o$  changes between **-10 V** and **+10 V** in your calculation.


**3.b)** Determine the value of  $R_1$  to obtain **1 kHz** oscillation frequency. Express period of the  $v_n$  waveform in terms of the  $\tau = R_1 C_1$  time constant and the peak values of  $v_n$  and  $v_o$ .

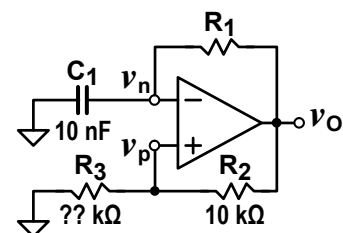**3.c)** Simulate the oscillator circuit with the calculated values by using **AD795** opamp model with **+/-12 V** supplies. Plot  $v_p$ ,  $v_n$  and  $v_o$ .



## Procedure

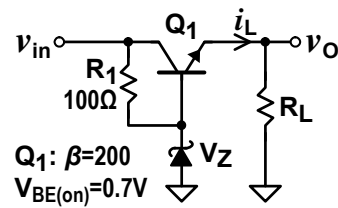1. Build the voltage regulator circuit given on the right using **BC237** or **BC238** as **Q1**. Initially connect a **10 k $\Omega$**  resistor in place of **R<sub>L</sub>**.



1.1 Determine line regulation when middle value of  $v_{in}$  is  $V_{inDC} = 6.0\text{ V}$ . Set  $v_{in} = 6.5\text{ V}$  and  $v_{in} = 5.5\text{ V}$  using the multimeter and measure  $v_O$  for both of the  $v_{in}$  settings. Repeat line regulation measurement when  $V_{inDC}$  is  $8.0\text{ V}$ . Compare your measurements with the simulation results.



$V_{inDC}$ value of $v_{in}$ (V)	$v_O$ (V) measured at $V_{inDC} + 0.5\text{V}$	$v_O$ (V) measured at $V_{inDC} - 0.5\text{V}$	line regulation (V/V)
6.0			
8.0			

1.2 Determine load regulation when  $R_L = 100\ \Omega$  is connected instead of  $10\text{ k}\Omega$  for  $v_{in} = 6.0\text{V}$  and  $v_{in} = 8.0\text{V}$ .

$V_{inDC}$ value of $v_{in}$ (V)	$v_O$ (V) measured for $R_L = 10\text{ k}\Omega$	$v_O$ (V) measured for $R_L = 100\ \Omega$	load regulation (mV/mA)
6.0			
8.0			

2. Build the **Wien bridge oscillator** given on the right. Set the DC supply output voltages using the multimeter to obtain **+12 V** and **-12 V** required for the opamp.

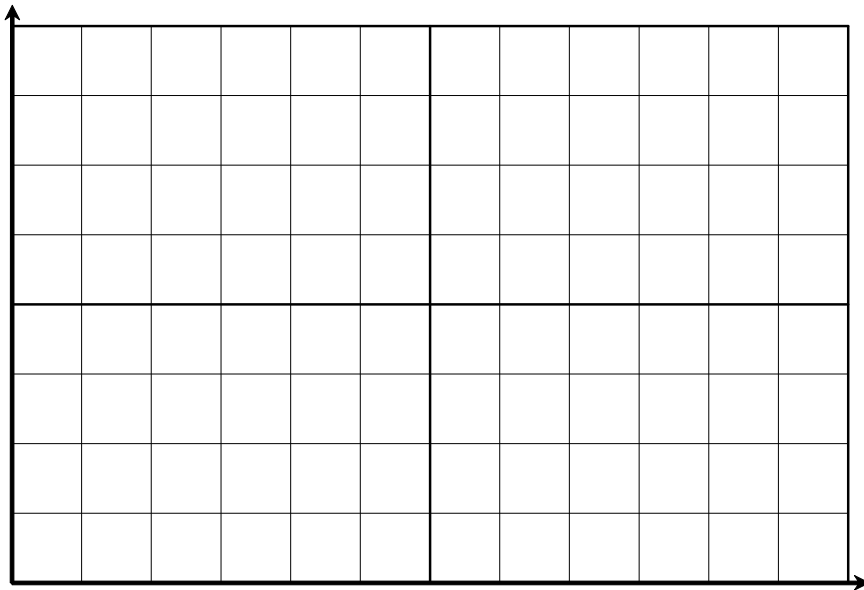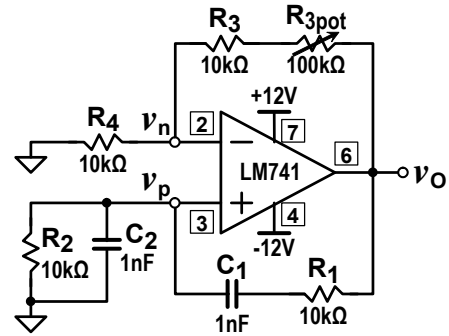2.1 Set  $R_{3pot} = 0 \Omega$  first, and then increase it just to the point where oscillations start at  $v_O$ . Plot  $v_n$ ,  $v_p$  and  $v_O$  waveforms below. Indicate units of amplitude and time axes on your plot. Measure and record the peak-to-peak output voltages and the oscillation frequency.



$v_n$  : \_\_\_\_\_  $v_p$  : \_\_\_\_\_  $v_O$  : \_\_\_\_\_  $F_{osc}$  = \_\_\_\_\_

2.2 Turn off DC supplies, disconnect and measure the resistance of  $R_3 + R_{3pot}$ . Does this result agree with your prediction in the preliminary work?



$R_3 + R_{3pot} =$  \_\_\_\_\_

2.3 Reconnect  $R_3 + R_{3pot}$  and measure the oscillation frequency obtained with the  $R_2$  resistance values listed in the following table. How does  $R_2$  affect the oscillation frequency? Compare your measurements with the frequency values obtained in the preliminary work.

$R_2$ (k $\Omega$ )	$F_{osc}$ (Hz)
10	
22	
33	
47	

3. Build the **Schmitt trigger oscillator** circuit given on the right. Use a standard resistor value closest to the  $R_3$  calculated in the preliminary work.

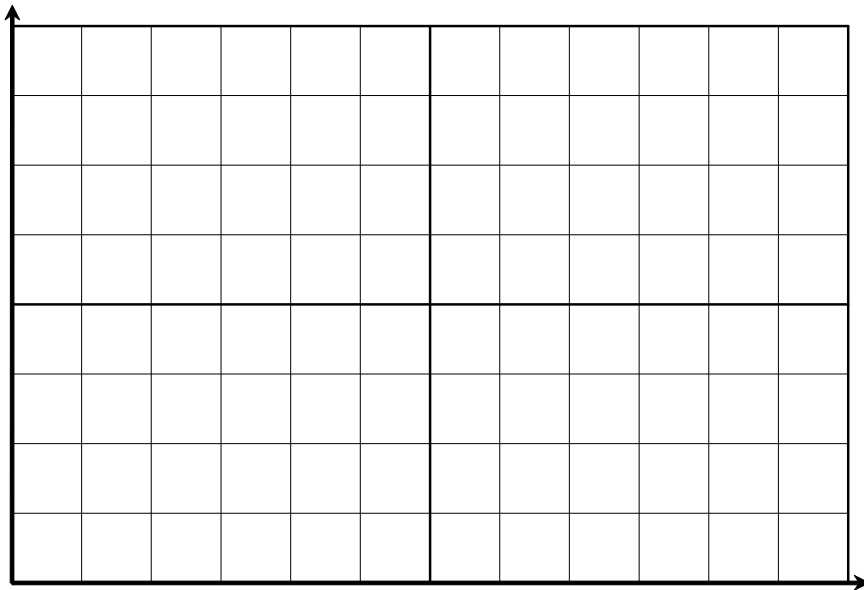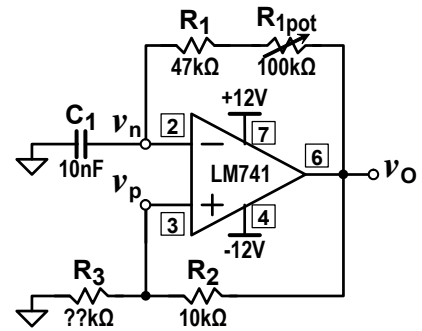3.1 Adjust  $100\text{ k}\Omega$   $R_{1\text{pot}}$  to obtain  $1\text{ kHz}$  oscillation frequency at  $v_O$ . Plot  $v_n$ ,  $v_p$  and  $v_O$  waveforms below indicating all critical amplitude and timing information. Compare your measurements with the results obtained in the preliminary work.



## Questions

**Q1.** List the steps in designing a Wien bridge oscillator.

**Q2.** List the steps in designing a Schmitt trigger oscillator.

**Q3.** Modify the circuit used in step-3 so that the opamp works with a single positive supply without significant change in the oscillation frequency.

**Hint:** Input waveforms should be centered around half the positive supply voltage. There is no DC level control on the negative opamp input. DC level of the positive opamp input depends on where **R<sub>3</sub>** is connected to.