

## EE315 - Electronics Laboratory

# Experiment - 3 Simulation

## BJT Transistor and DC Biasing

### Preliminary Work

- For the circuit given in Figure 1
  - Calculate the value of  $R_{adj}$  that makes  $V_{CE}$  equal to 5 V.
  - Calculate  $V_{RB}$  (voltage drop across  $R_B$ ).
  - Explain the reason for choosing  $V_{CE}$  equal to 5 V.

 


Figure 1. Emitter-stabilized bias circuit

- For the circuit given in Figure 2, determine  $I_B$ ,  $I_C$ ,  $V_B$ ,  $V_E$ , and  $V_{CE}$ .

 


Figure 2. Voltage divider biasing circuit

- For the circuit given in Figure 3, derive an expression for  $v_O = v_C$  as a function of  $v_{drv}$ . Specify the  $v_{drv}$  levels where the transistor turns off completely ( $i_C = 0$ ) and it goes into saturation ( $i_C < \beta i_B$ ).

 


Figure 3. Switching circuit

- For the circuit given in Figure 4, find the values of  $R_C$  and  $R_B$ , so that  $I_{Csat} = 2 \text{ mA}$  and  $v_O$  changes between 10 V and 0 V while  $v_{drv}$  is a 1 kHz square wave signal switching between 0 V and 10 V. Draw  $v_{drv}$  and  $v_O$  as a function of time.

 


Figure 4. Switching circuit

## Procedure

### 1. Build the circuit given in Figure 1.

Place an NPN transistor on the schematic and select **BC547B** as the transistor model (right-click on the transistor figure and click on "Pick New Transistor").

You will use the same transistor model for all parts of the experiment.

Place a normal resistor as  $R_{adj}$  change its value until you obtain  $V_{CE} = 5\text{ V}$  with less than 1% error.

$$R_{adj} =$$

**1.a)** Measure  $V_{BE}$  and the voltages across  $R_B$ , and  $R_C$  while  $V_{CE}$  is still at **5 V**. Also measure  $I_B$ ,  $I_C$ , and  $\beta$ .

$$V_{BE} =$$

$$V_{RB} =$$

$$V_{RC} =$$

$$I_B =$$

$$I_C =$$

$$\beta =$$

**1.b)** Change every one of the resistance values  $R_B$ ,  $R_C$ ,  $R_E$ , and transistor parameters  $\beta$ , and  $V_{BE(on)}$  by 1% and record the new  $I_C$  values in the following table. Change only one of the resistor values or parameters at a time and keep the others at their original settings for each  $I_C$  measurement.

| changed component | new value of $I_C$ (mA) | percent change in $I_C$ |
|-------------------|-------------------------|-------------------------|
| $R_B$             |                         |                         |
| $R_C$             |                         |                         |
| $R_E$             |                         |                         |
| $\beta$           |                         |                         |
| $V_{BE(on)}$      |                         |                         |

**1.c)** Which value(s) among  $R_B$ ,  $R_C$ ,  $R_E$ ,  $\beta$ , and  $V_{BE(on)}$  has/have the most significant effect on  $I_C$ ?

**2.a)** Build the circuit in Figure 2. Measure the values of  $I_B$ ,  $I_C$ ,  $V_B$ ,  $V_{BE}$ , and  $V_{CE}$ .

$$I_B =$$

$$I_C =$$

$$\beta =$$

$$V_B =$$

$$V_{BE} =$$

$$V_{RC} =$$

**2.b)** In practice, all component values are specified with a tolerance range. Tolerance range determines the minimum and maximum of the actual values that will be obtained if several of these components are tested. For example, a **100 k $\Omega$**  resistor with **5 %** tolerance may have an actual value between **95 k $\Omega$**  and **105 k $\Omega$** . Similarly, the minimum and maximum values of  **$\beta$**  are given in transistor datasheets.

If thousands of this circuit are to be manufactured, then you had to make sure that  **$V_{CE}$**  will be reasonable within the tolerance range of all components. Indicate in the table below, which end ("**min**" or "**max**") of the tolerance range should be used for each parameter in calculation of the lowest and highest values of  **$V_{CE}$** .

| component or parameter         | For lowest $V_{CE}$ | For highest $V_{CE}$ |
|--------------------------------|---------------------|----------------------|
| <b><math>R_1</math></b>        |                     |                      |
| <b><math>R_2</math></b>        |                     |                      |
| <b><math>R_C</math></b>        |                     |                      |
| <b><math>R_E</math></b>        |                     |                      |
| <b><math>\beta</math></b>      |                     |                      |
| <b><math>V_{BE(on)}</math></b> |                     |                      |

**3.a)** Build the circuit given in Figure 3. Use a pulse waveform as  $v_{drv}$  that changes from **0 V** to **10 V** in **1 ms** (i.e. PULSE(0 10 0 1m 1u 1m 3m)).


**3.b)** Measure the range of  $v_{drv}$  values in which the transistor acts as a switch.

$v_{drv-Low-Max} =$  (where  $v_o > 90\%$  of  $V_{CC}$ )

$v_{drv-High-Min} =$  (where  $v_o < 10\%$  of  $V_{CC}$ )

**4.a)** Setup the circuit in Figure 4 using the  $R_B$  and  $R_C$  values previously calculated in the preliminary work. Set  $v_{drv}$  source timing parameters to obtain a **10 kHz** pulse signal with **50 %** duty cycle (i.e. `PULSE(0 10 0 1u 1u 49u 100u)`). Keep the  $v_{drv}$  source **Trise** and **Tfall** settings at **1  $\mu$ s** all the time. Set simulation time long enough to observe the steady state  $v_O$  waveform. Change the peak voltage of  $v_{drv}$  as in the following table and record the peak-to-peak  $v_O$  voltage.

| Freq. (kHz) | $v_{drv}$ (Vpeak) | $v_O$ (Vp-p) |
|-------------|-------------------|--------------|
| 10          | 2                 |              |
|             | 4                 |              |
|             | 6                 |              |
|             | 8                 |              |
|             | 10                |              |
|             | 2                 |              |
|             | 4                 |              |
|             | 6                 |              |
|             | 8                 |              |
|             | 10                |              |

 

**4.b)** Set  $v_{drv}$  peak voltage to **10 V** and increase  $v_{drv}$  frequency (reduce **Ton** and **Tperiod**) until the peak-to-peak  $v_O$  voltage decreases down to **5 V** roughly. Make sure that duty cycle of the  $v_{drv}$  remains as **50%** while the **Trise** and **Tfall** settings are **1  $\mu$ s** all the time. Measure  $v_O$  for the other  $v_{drv}$  peak voltage settings and record the results in the table above. Plot  $v_O$  amplitude (**Vp-p**) versus  $v_{drv}$  (**Vpeak**) for the two frequency settings.

**4.c)** Comment on the difference in the output signals resulting from the changes in  $v_{drv}$  peak voltage and frequency.