

EE315 - Electronics Laboratory

Experiment - 5

MOSFET Characteristics and Small Signal Amplifier

Preliminary Work

1. The inverter in Figure 1 utilizes an N-channel enhancement-mode MOSFET with the parameters $K_n = 1 \text{ mA/V}^2$ and $V_{TN} = 2 \text{ V}$. Find the inverter output at v_{out} when $v_{in} = 3 \text{ V}$ and $v_{in} = 4 \text{ V}$. Plot the v_{in} - v_{out} transfer characteristics of the inverter.

Equations for the N-channel MOSFET are given below.

$$i_D = K_n(v_{GS} - V_{TN})^2 \quad (\text{in SAT region: } v_{DS} \geq v_{GS} - V_{TN})$$

$$i_D = K_n[2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2] \quad (\text{in triode=non-SAT region: } v_{DS} < v_{GS} - V_{TN})$$

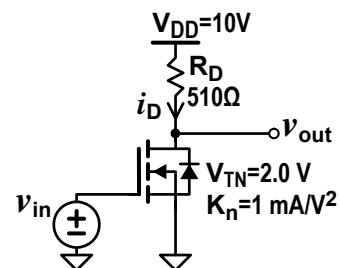


Figure 1

2. Consider the MOSFET amplifier in Figure 2 with the parameters $K_n = 1 \text{ mA/V}^2$ and $V_{TN} = 2 \text{ V}$. Determine the resistor values to obtain roughly $I_D = 1 \text{ mA}$ and to set V_D approximately midway between V_{DD} and V_G .

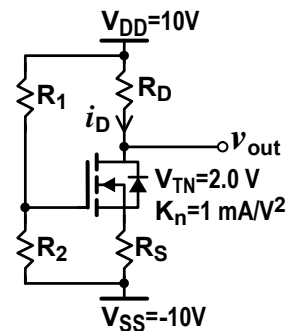


Figure 2

Procedure

1.a) Build the inverter circuit given in Figure 1 using $R_D = 510\ \Omega$ and $V_{DD} = 10\text{ V}$. Initially set $v_{in} = 0\text{ V}$.

1.b) Increase v_{in} gradually until the point v_{out} becomes constant. Record the v_{in} and v_{out} values to identify significant changes in the inverter response.

2.a) Build the circuit in Figure 3. Apply an input voltage varying between 0 V and 10 V setting $v_{in} = 5\text{ V} + 5\text{ V} \sin(2000\pi t)$.

2.b) Connect the oscilloscope probes as shown in Figure 3. Observe and record the i_D versus v_{GS} plot using the oscilloscope in X-Y mode. Note that, polarities of v_{GS} and i_D are reversed on the oscilloscope screen.

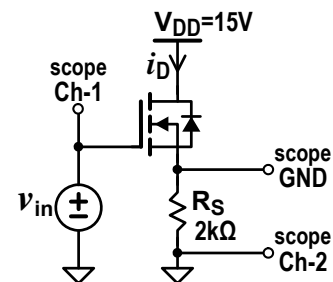


Figure 3

3.a) Build the circuit in Figure 4 using the resistor values you calculated in the preliminary work. Set v_{in} frequency to 10 kHz and amplitude to 10 mV . You may need a higher amplitude to obtain significant results when you begin the measurements.

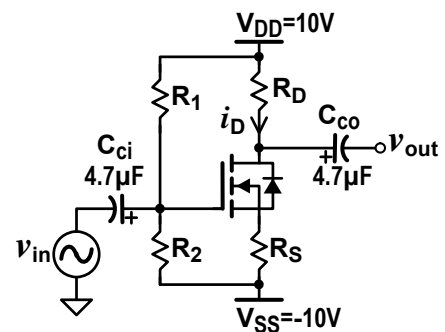


Figure 4

3.b) Display input and output signals on the oscilloscope and observe the phase shift. Measure the output voltage, phase shift and calculate the voltage gain.

3.c) Connect a $100\text{ k}\Omega$ resistor between the input voltage source and the coupling capacitor, C_{ci} . Measure the voltage gain and use the results from step 3.b to deduce the amplifier input resistance, R_{in} .

3.d) Measure the output resistance, R_o , of the amplifier.