

## EE315 - Electronics Laboratory

# Experiment - 4 Simulation

## BJT Small Signal Analysis

### Preliminary Work

**1.a)** Calculate  $A_v$ ,  $A_i$ ,  $R_{in}$ , and  $R_{out}$  on the circuit given in Figure 1. Assume that  $C_{Ci}$  and  $C_{Co}$  behave as open circuit for DC signals and as short circuit for AC signals.

**1.b)** Determine limits of the signal source,  $v_s$ , for the transistor to remain in forward-active region.

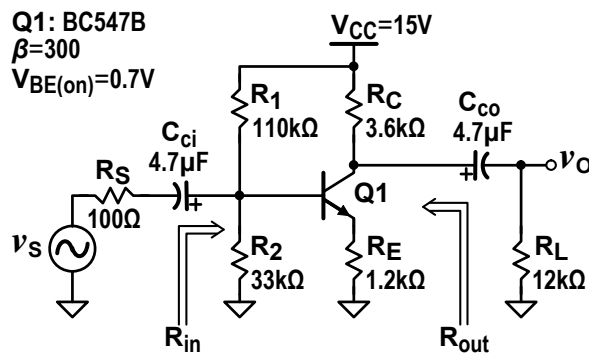


Figure 1. Common-emitter amplifier

**2.a)** Calculate  $A_v$ ,  $A_i$ ,  $R_{in}$ , and  $R_{out}$  on the circuit given in Figure 2. Assume that the coupling capacitors,  $C_{Ci}$  and  $C_{Co}$ , behave as open circuit for DC signals and as short circuit for AC signals.

**2.b)** Determine limits of the signal source,  $v_s$ , for the transistor to remain in forward-active region. (Hint: AC current on  $R_L$  will be added onto the quiescent emitter current.)

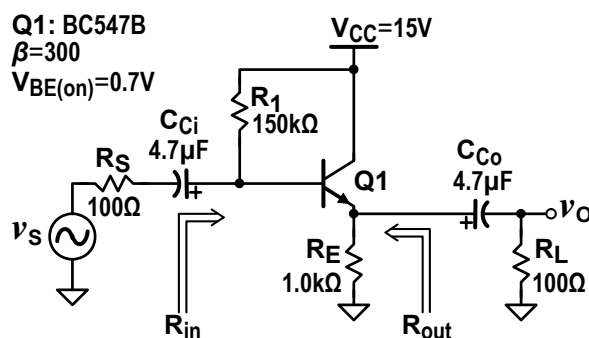


Figure 2. Common-collector amplifier (emitter follower)

## Procedure

1. Build the circuit given in Figure 1 and select **BC547B** as the transistor model. Set the **value** of the voltage source  $v_s$  to obtain **1 kHz** sine wave, with **2 Vp-p** amplitude. Select a **4.7  $\mu$ F Al electrolytic** capacitor model (right-click on the capacitor figure and click on "Select Capacitor"). Note the polarity of the capacitors on the circuit diagram.

1.a) Measure the voltage gain,  $A_v$ .

$$V_{Sp-p} = \quad V_{Op-p} = \quad A_v =$$

1.b) Determine the current gain,  $A_i$ , by measuring the current through  $R_S$  and  $R_L$ .

$$I_{Sp-p} = \quad I_{Lp-p} = \quad A_i =$$

1.c) Disconnect  $R_L$  and measure the input resistance,  $R_{in}$ .

$$V_{Sp-p} = \quad I_{Sp-p} = \quad R_{in} =$$

1.d) Measure peak-to-peak output voltage while  $R_L$  is disconnected. Connect  $R_L$  and change its value to obtain half the output voltage measured without any load that will give the  $R_{out}$  of the amplifier.

$$V_{Op-p(NoLoad)} = \quad R_{out} =$$

1.e) Find the maximum peak  $v_s$  amplitudes before the transistor goes into cut-off or saturation. Compare the results with your calculations in the preliminary work.

$$V_{Speak(cut-off)} = \quad V_{Speak(sat)} =$$

1.f) Connect a **4.7  $\mu$ F** capacitor in parallel to  $R_E$ . Make sure that the polarity of the capacitor matches the DC voltage polarity on  $R_E$ . Measure the voltage gain,  $A_v$ , again as described in step 1.a.

$$V_{Sp-p} = \quad V_{Op-p} = \quad A_v =$$

1.g) Draw the small signal model of the common-emitter amplifier with the capacitor in parallel to  $R_E$ , and calculate the voltage gain,  $A_v$ , based on your model.

**2.** Build the emitter-follower circuit given in Figure 2. Verify that the voltage source output is set to **1 V<sub>p-p</sub>**, **1 kHz**, and repeat the steps **1.a**, **1.b**, and **1.c** for this circuit

**2.a)** Measure the voltage gain, **A<sub>v</sub>**.

$$V_{Sp-p} = \quad V_{Op-p} = \quad A_v =$$

**2.b)** Determine the current gain, **A<sub>i</sub>**.

$$I_{Sp-p} = \quad I_{Lp-p} = \quad A_i =$$

**2.c)** Disconnect **R<sub>L</sub>** and measure the input resistance, **R<sub>in</sub>**.

$$V_{Sp-p} = \quad I_{Sp-p} = \quad R_{in} =$$

**2.d)** Increase **v<sub>S</sub>** amplitude to **2.0 V<sub>p-p</sub>** and observe **v<sub>O</sub>** waveform. How do you explain the distortion in the **v<sub>O</sub>** waveform?

**2.e)** Find a way to restore the **v<sub>O</sub>** waveform while keeping **v<sub>S</sub>** amplitude at **2.0 V<sub>p-p</sub>**, and **R<sub>L</sub> = 100 Ω**. Explain how you can restore the **v<sub>O</sub>** waveform.

**2.f)** Measure the output resistance, **R<sub>out</sub>** using the method discribed in step **1.d**. Make sure that the output waveform is not distorted while you measure **R<sub>out</sub>**.

$$V_{Op-p(NoLoad)} = \quad R_{out} =$$