

**EE315 - Electronics Laboratory**  
**Experiment - 6 Simulation**  
**BJT Differential Amplifier**

Name : Emre Nedim Hepsağ

Number : 250206012

Submission Date: 14/12/2020

**Preliminary Work**

$$I_a \Rightarrow \beta \approx \beta + 1 \Rightarrow I_C \approx I_E \approx I_Q :$$

$$2.4k \times I_C + 0.7 + 100 \times I_E = 12$$

$$I_Q = I_C = I_E = \frac{12 - 0.7}{2.4k + 100} = \underline{\underline{4.52 \text{ mA}}}$$

$$I_b \Rightarrow 2.4k \times I_{CQ3} + V_{BEQ3} + 100 \times I_{EQ3} = 12$$

$$- 2.4k \times I_{CQ4} + V_{BEQ4} + 100 \times I_{EQ4} = 12$$

$$V_{BEQ3} + 100 \times I_{BQ3} \times \beta_{Q3} = V_{BEQ4} + 100 \times I_{BQ4} \times \beta_{Q4}$$

$$c \Rightarrow \text{If } \beta_{Q3} > \beta_{Q4} \Rightarrow I_{BQ4} > I_{BQ3}$$

$$\text{However, } 100 \times I_{BQ3} \times \beta_{Q3} = 100 \times I_{BQ4} \times \beta_{Q4} \Rightarrow I_{Q3} = I_{Q4}$$

Thus,  $I_Q$  does not change.

$$c' \Rightarrow \text{If } V_{BEQ3} > V_{BEQ4} \Rightarrow 100 \times I_{BQ3} \times \beta_{Q3} < 100 \times I_{BQ4} \times \beta_{Q4}$$

Thus,  $I_{Q3} < I_{Q4}$ ,  $I_Q$  would increase.

**1.c)** Describe an experiment to measure the output resistance of the current mirror.

>> We can do the same thing as 1c in procedure to measure the output resistance. If we add a test AC voltage after load resistance, the current mirror circuit act as an independent DC current source. Thus, AC voltage creates an AC current and AC voltage in the circuit. If we divide the AC voltage difference to AC current on the circuit, we can find the output resistance of the current mirror circuit.

## Results

1. Build the current mirror circuit given in Figure 1 and select **BC547B** as the transistor model. You will use the resistor values specified for  $R_L$  in step-1.a.

1.a) Measure the DC current output  $I_Q$  of the current mirror for the following values of  $R_L$ .

$R_L$ used	$I_Q$ (mA)
<b>750 <math>\Omega</math></b>	4.5280725mA
<b>1.5 k<math>\Omega</math></b>	4.5140141mA
<b>2.2 k<math>\Omega</math></b>	4.50027mA
<b>3.3 k<math>\Omega</math></b>	3.5069648mA

1.b) Explain any major change in the DC current output  $I_Q$ .

>>When we have 2.2k ohm  $R_L$ , we observe  $I_Q$  as 4.5mA and  $V_{CE}$  as 1.65V. On the other hand, when we have 3.3k ohm  $R_L$ , we observe  $I_Q$  as 3.5mA and  $V_{CE}$  as 31.35mV. It means that, because of high resistance of  $R_L$ , it draws higher values and this result in lack of voltage on  $V_{CE}$  to make the transistor in forward active region. Thus, we can deduce that, when we have 3.3k ohm  $R_L$ , transistor gets into saturation region and  $I_{CQ4}$  becomes less than beta times  $I_{BQ4}$ .

1.c) Apply an AC test signal, and measure the AC voltage and current at the current mirror output to find the current source output resistance. Use  $R_L=1.5 \text{ k}\Omega$ , and set the function generator to obtain 4 Vp-p sinusoidal test source  $v_{tst}$  as shown in Figure 3.

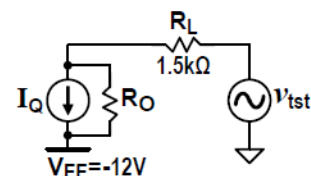


Figure 3. Test setup to measure current source output resistance

Find the output resistance  $R_O$  of the constant current source model at the frequency settings specified for  $v_{tst}$  in the following table.

Frequency values in **MHz** range can be entered with the **Meg** scaling factor in LTspice. For example, **3 MHz** frequency setting for a sinusoidal source can be written as "3Meg" or "3000k".

$v_{tst}$ frequency	$v_{RL}$ (mVp-p)	$R_O$ (k $\Omega$ )	$V_{Ro}(V_{p-p})$	$I_{Ro}(uA_{p-p})$
<b>10 kHz</b>	29.260654	232.852	3.9623	17.016
<b>30 kHz</b>	56.026762	231.496	3.9660	17.132
<b>100 kHz</b>	133.67936	206.280	3.9575	19.185
<b>300 kHz</b>	126.75296	127.957	3.9549	30.943
<b>1 MHz</b>	213.23238	45.334	3.9496	87.121
<b>3 MHz</b>	464.05871	15.384	3.9174	254.626

>>To find  $R_O$  I divide  $V_{Ro\_ACp-p}$  with  $I_{RL\_ACp-p}$ . That gave us the small signal resistance of the current mirror which is  $R_O$ .

**1.d)** If this current mirror is used for biasing a differential amplifier, how should the CMRR change depending on the frequency of the common-mode input? Why?

>>Common mode rejection ratio is the rate of differential mode gain over the common mode gain. And the common mode gain is dependent to  $R_o$  of the current mirror circuit. The higher  $R_o$  results in less common mode gain. Thus, we can say that, if we have higher frequency, we would have lower  $R_o$ , and this results greater

$$A_d = \frac{\beta R_C}{2(r_\pi + R_B)} \quad \text{So} \quad A_d = \frac{\beta R_C}{2(r_\pi + R_B)} \quad \text{For} \quad A_d = \frac{\beta R_C}{2(r_\pi + R_B)} \quad \text{to be as high as} \quad \text{CMRR and the}$$

$$A_d = \frac{\beta R_C}{2(r_\pi + R_B)} \quad A_{cm} = \frac{-\beta R_C}{r_\pi + R_B + 2(1 + \beta)R_o}$$

$$\text{CMRR} = \left| \frac{A_d}{A_{cm}} \right|$$

# Conclusion

>>In this experiment, firstly we observed the effect of  $R_L$  on  $I_Q$  and we figured out that when  $R_L$  is high enough to make transistor in saturation, we see dramatic difference.

Secondly, to observe the output resistance of the current mirror circuit, we sat an experiment and found out output resistance in difference frequency. We saw that the higher the frequency is, the lower the output resistance.

Finally, we figured out the effect of frequency on the common mode input and CMRR. We conclude that there is an inverse proportion on them.